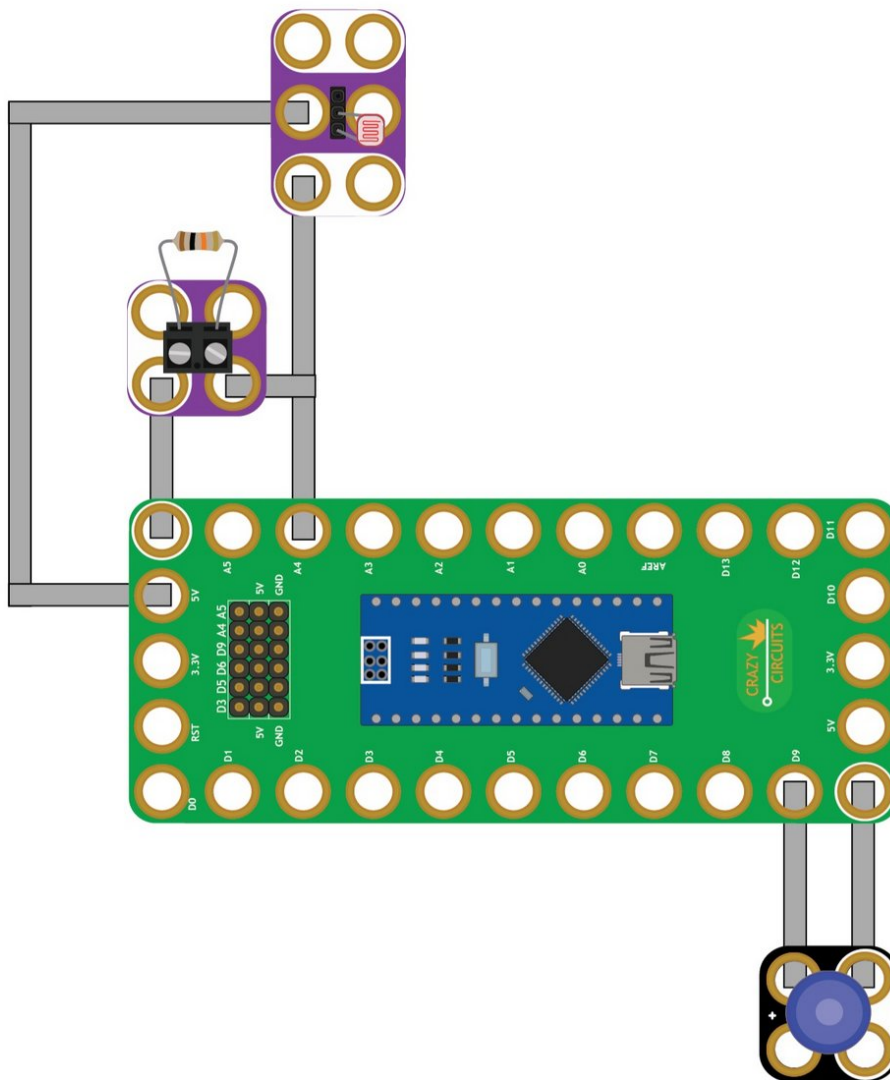




## 07 - Light Dependent Resistor with LED

Use our Programming 101 kit to control an LED with a light dependent resistor.

Written By: Pete Prodoehl



# INTRODUCTION

Use our Robotics Board to control an LED with a light dependent resistor.



## TOOLS:

- [Scissors](#) (1)
- [Computer](#) (1)
- [Slotted Screwdriver](#) (1)




## PARTS:

- [Crazy Circuits Robotics Board](#) (1)
- [Light Dependent Resistor](#) (1)
- [10K Ohm Resistor](#) (1)
- [Female Header Chip](#) (1)
- [Crazy Circuits Screw Terminal Chip](#) (1)
- [Crazy Circuits LED Chip](#) (1)
- [Maker Tape](#) (1)


1/8" Wide

## Step 1 — Build the Circuit

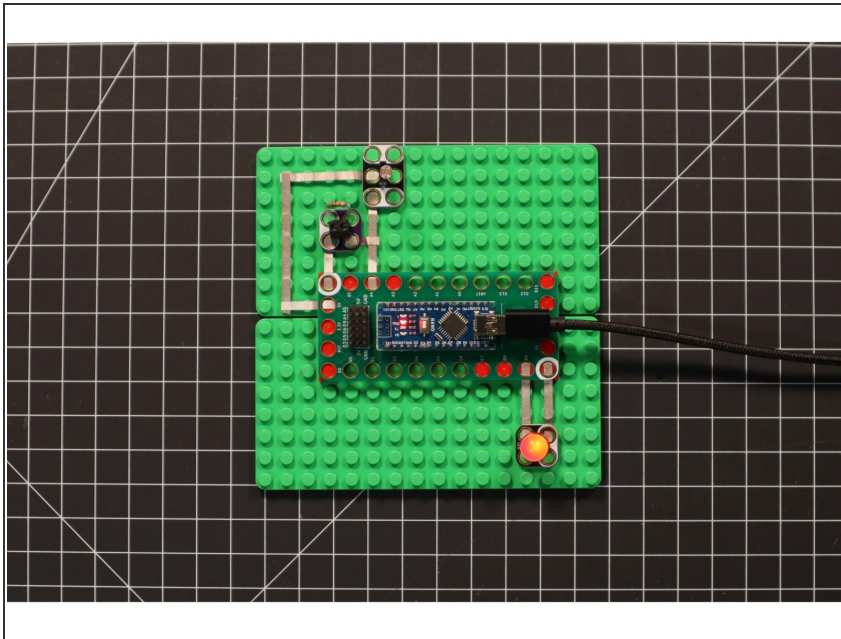

- Build the circuit as shown in the diagram using the components specified.
- ❗ The light dependent resistor can be inserted into two of the pin sockets on the Female Header component.
- ❗ The standard resistor can be inserted into the Screw Terminal component. (You'll need a small screwdriver to tighten the connectors.)

## Step 2 — Upload the Code

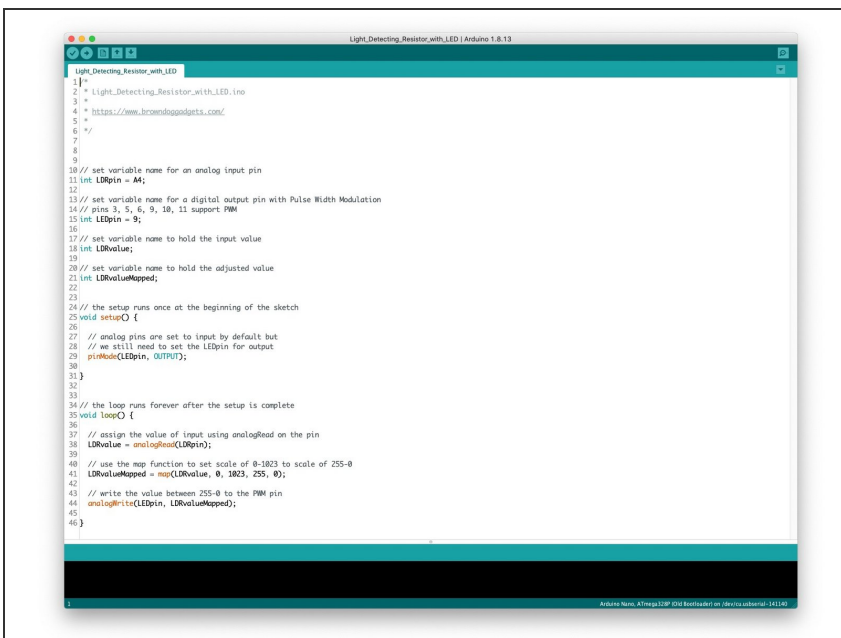

- Upload the Arduino sketch to the Robotics Board.
- You can find the code here:  
<https://github.com/BrownDogGadgets/Progr...>