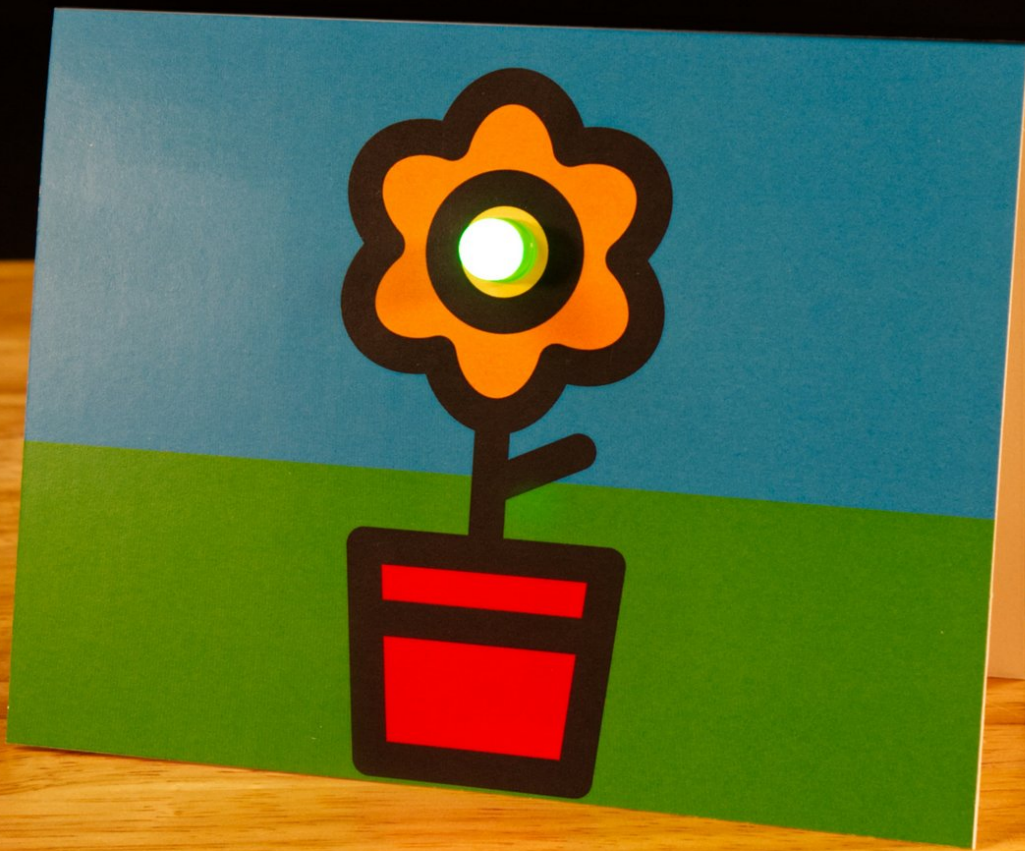




Mother's Day Flower Card

Create a fun light-up card for Mother's Day. Just add an LED, a CR2032 battery, and some Maker Tape.

Written By: Pete Prodoehl



INTRODUCTION

Create a fun light-up card for Mother's Day. Just add an LED, a CR2032 battery, and some Maker Tape.

You can make this project (and many more!) with our **Paper Circuits Kit**.



TOOLS:



- [Scissors](#) (1)



PARTS:

- [Paper Circuits Kit](#) (1)

Step 1 — Make Your Card

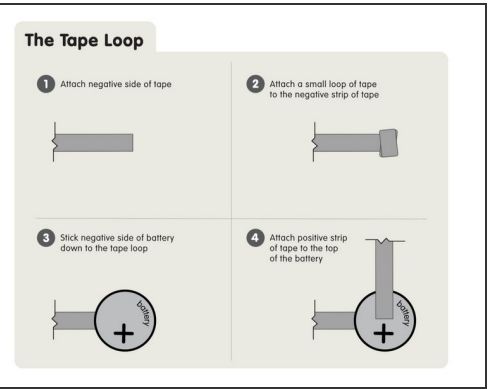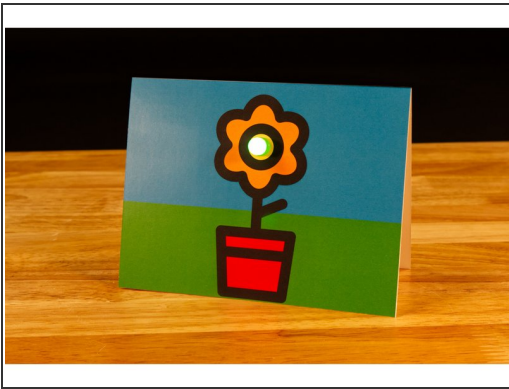

- In general build this project in this order:
 - Print out the full-color card, or print out the black and white card, and color/decorate as desired.
 - Poke holes through front for LED legs, then push legs through front.
 - On inside of card, bend legs down flat against paper.
 - Add Maker Tape and battery to complete your circuit.
- ① Note: If you are using thicker paper (such as cardstock) we recommend using a large safety pin to poke the holes in the paper to put the LED legs through.

Enjoy your card!