



# Halloween Pumpkin Card

Create a light-up card featuring a Halloween Pumpkin! Just add two LEDs, a CR2032 battery, and some Maker Tape.

Written By: Pete Prodoehl



## INTRODUCTION

Create a light-up card featuring a Halloween Pumpkin! Just add two LEDs, a CR2032 battery, and some Maker Tape.

There's a full-color version as well as a black & white version that makes a great coloring activity.

You can make this project (and many more!) with our **Paper Circuits Kit**.



### TOOLS:

- [Scissors](#) (1)
- [Safety Pin](#) (1)

*Optional*

- [Pushpin](#) (1)


*Optional*



### PARTS:

- [Paper Circuits Kit](#) (1)

## Step 1 — Make Your Card

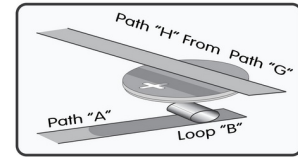

### Tape Loop Area

Tape Loop "B" placed atop left end of path "A".  
Battery (+ side up) on top of Tape Loop.  
Path "H" stuck atop Battery from path "G".

- This paper circuits card is a great beginner project. Just follow the steps below to make your card.
- Print out the full-color card, or print out the black and white card and color/decorate as desired.
- Poke holes through the front of the card for the LED legs, then push the legs through the front.
- ☑ Make note of where the positive and negative legs go. Polarity matters!
  - On the inside of the card, bend the LED legs down flat against the paper.
  - Add Maker Tape and a battery to complete your circuit.
- ⓘ Note: If you are using thicker paper (such as cardstock) we recommend using a large safety pin to poke the holes in the paper to put the LED legs through.

Enjoy your card!