




Day 4: Circuits That Sense: Intro to Photo

Resistors

Broaden understandings of control in circuitry by using a photo resistor as a sensor within a light circuit. Use focused observation to deduce how it works!

Written By: Andy Wallus

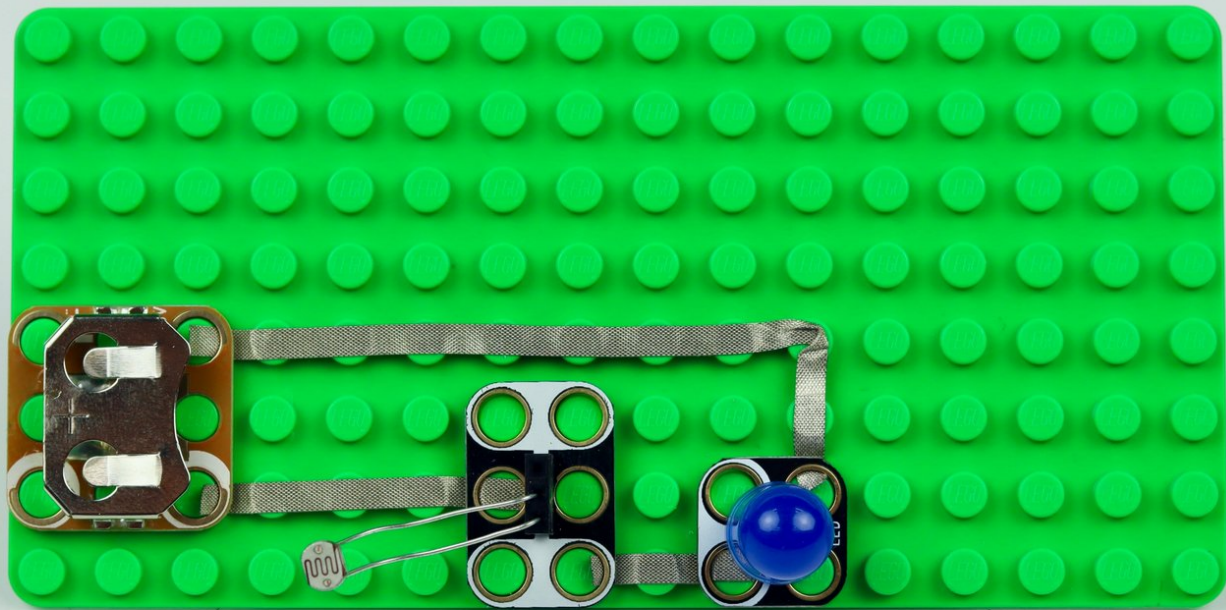



TOOLS:

- [Crazy Circuits Classrooms: Circuits 101](#) (1)
- [Scissors](#) (1)

After today, your students will understand that some resistors can have a range of changeable resistances. They will apply these understandings while using a photo resistor within their circuitry as a sensor.